 


Name _____

Date _____

Simple Circuits: What Works?

Draw diagrams of the configurations that worked to light the bulb using the battery and the wire. Make sure it's clear which end of the battery is which and exactly where you are attaching the wire.



Draw diagrams of configurations that did NOT work to light the bulb using the battery and the wire.

