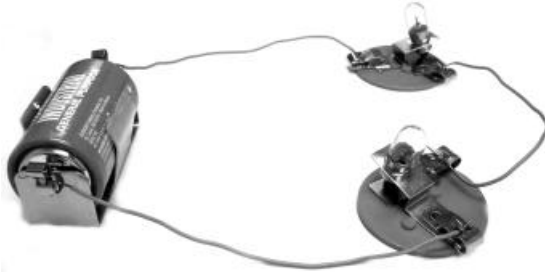


Investigating Series and Parallel Circuits

Name _____ Date _____

Set up the circuits pictured below and record your observations.

Series Circuit (bulbs in series)




- 1) What happens? _____
- 2) Do both bulbs light up? _____
- 3) Are there any differences in how bright they are compared to each other?

....compared to when there is only one bulb in a circuit? _____

- 4) If you remove one of the bulbs, does the other one still light up? _____

Draw a diagram showing what you think is going on at the level of electrons and protons to make the bulb light.

Parallel Circuit (bulbs in parallel)

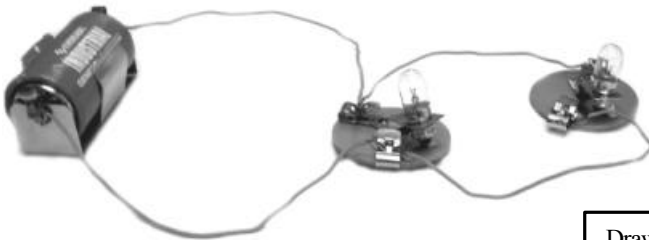

- 1) What happens? _____
- 2) Do both bulbs light up? _____
- 3) Are there any differences in how bright they are compared to each other?


....compared to when there is only one bulb in a circuit? _____

- 4) If you remove one of the bulbs, does the other one still light up? _____

Draw a diagram showing what you think is going on at the level of electrons and protons to make the bulb light.

Investigating Series and Parallel Circuits

Series Circuit (batteries in series)

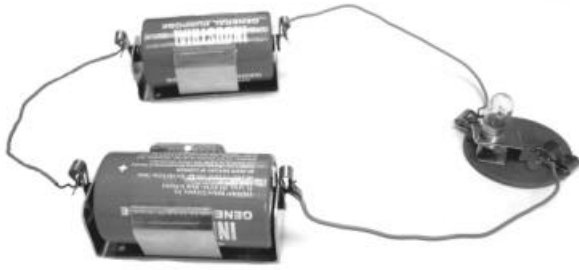

- 1) Does the bulb light? _____
- 2) Are there any differences in how bright the bulb is compared to when there is only one battery in a circuit?

- 3) If you remove one of the batteries, does the bulb still light up? _____

Draw a diagram showing what you think is going on at the level of electrons and protons to make the bulb light.

Parallel Circuit (batteries in parallel)



- 1) Does the bulb light? _____
- 2) Are there any differences in how bright the bulb is compared to when there is only one battery in a circuit?

- 3) If you remove one of the batteries, does the bulb still light up? _____

Draw a diagram showing what you think is going on at the level of electrons and protons to make the bulb light.