


## **Analogies for Analyzing Series and Parallel Circuits**

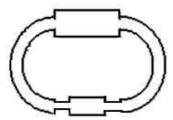
## **Basic Model for Series and Parallel Circuits**



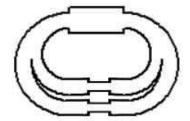

## Cars on a Highway Analogy

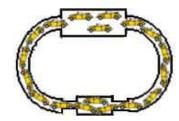

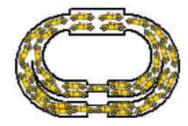

## Water in a Hose Analogy

